



Report on LAB 2

(Topics in Adv Comp Eng: Embedded Systems Hardware EE 493)

NAME: Prince K. Bose

NET ID: pkb44

RUID: 186008149

DATE: 3/7/19

Purpose

The main purpose of this lab was to build a 4 bit, 16 function ALU from ground up. In the pre-lab we were introduced to a concept similar to abstraction/ classes in programming. Here, we created a 1 bit adder once, then used 4 different instances of the same adder to create a 4 bit ripple carry adder.

There are 4 main components to the circuit of Lab 2:

1. Debounce Switch
2. MY_ALU
3. ALU_Tester

PRE LAB

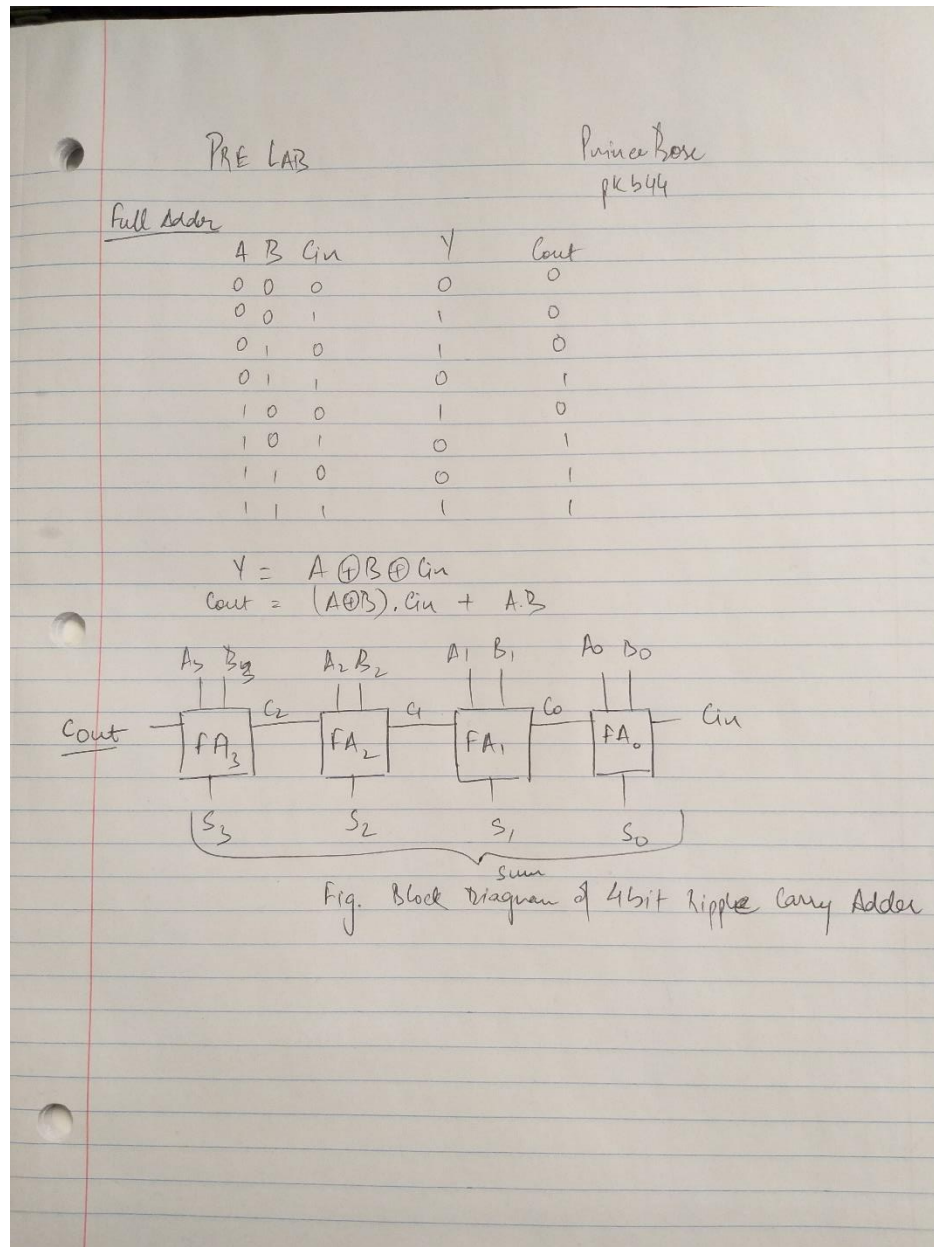


Fig. 1 : Pre Lab Working

1 Bit Adder

The 1 bit adder has 3 inputs A, B and Cin and produces 2 outputs S and Cout. The Truth Table is as shown in Figure 1.

VHDL CODE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Adder_1bit is
Port ( Cin : in std_logic;
      A : in std_logic;
      B : in std_logic;
      Sumout : out std_logic;
      Cout: out std_logic);
end Adder_1bit;
```

```
architecture Behavioral of Adder_1bit is
begin
```

```
Sumout <= A xor B xor Cin;
Cout <= (((A xor B) and Cin) or (A and B));
```

```
end Behavioral;
```

SCHEMATIC

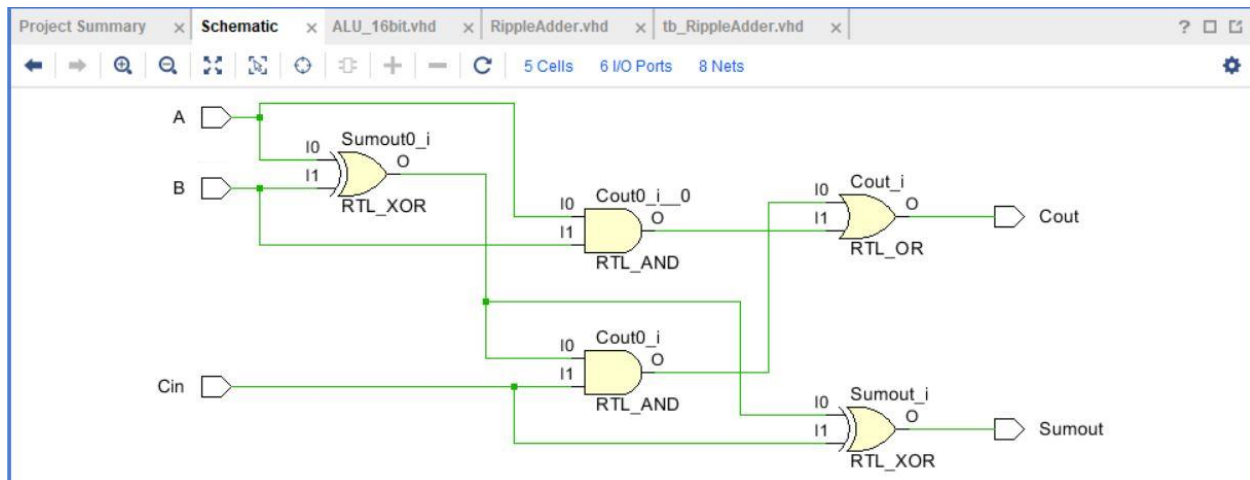


Fig. 2: 1 Bit Adder Schematic

Ripple Carry Adder

The ripple carry adder has a functional block diagram as shown in Figure 1.

It basically cascades four 1 bit adders, Cout of each stage is passed on to the input of the next stage.

VHDL CODE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity RippleAdder is
  Port ( A : in std_logic_vector (3 downto 0);
        B : in std_logic_vector (3 downto 0);
        Cin: in std_logic;
        Cout : out std_logic;
        S : out std_logic_vector (3 downto 0));
end RippleAdder;
```

architecture Behavioral of RippleAdder is

```
component Adder_1bit
  Port ( Cin : in std_logic;
        A : in std_logic;
        B : in std_logic;
        Sumout : out std_logic;
        Cout: out std_logic);
end component;
```

```
signal c1,c2,c3 : std_logic;
```

```
begin
```

```
FA0: Adder_1bit
  Port map( Cin => Cin,
            A => A(0),
            B => B(0),
            Sumout => S(0),
            Cout => c1);
```

```
FA1: Adder_1bit
  Port map( Cin => c1,
            A => A(1),
            B => B(1),
            Sumout => S(1),
```

```
Cout => c2);
```

```
FA2: Adder_1bit
```

```
Port map( Cin => c2,
          A => A(2),
          B => B(2),
          Sumout => S(2),
          Cout => c3);
```

```
FA3: Adder_1bit
```

```
Port map( Cin => c3,
          A => A(3),
          B => B(3),
          Sumout => S(3),
          Cout => Cout);
```

```
end Behavioral;
```

VHDL TESTBENCH

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity tb_RippleAdder is
end tb_RippleAdder;
```

```
architecture Behavioral of tb_RippleAdder is
component RippleAdder
Port ( A : in std_logic_vector (3 downto 0);
      B : in std_logic_vector (3 downto 0);
      Cin: in std_logic;
      Cout : out std_logic;
      S : out std_logic_vector (3 downto 0));
end component;
```

```
signal tb_A : std_logic_vector(3 downto 0) := "0101";
signal tb_B : std_logic_vector(3 downto 0) := "1010";
signal tb_C : std_logic := '0';
signal S : std_logic_vector(3 downto 0) := "0000";
signal Cout : std_logic;
```

```
begin
```

```
inputgen: process
```

```
begin

wait for 100 ns;
tb_A <= "0000";
tb_B <= "0001";
tb_C <= '0';

wait for 100 ns;
tb_A <= "1000";
tb_B <= "0101";
tb_C <= '1';

wait for 100 ns;
tb_A <= "1111";
tb_B <= "0100";
tb_C <= '1';

wait for 100 ns;
tb_A <= "0000";
tb_B <= "0000";
tb_C <= '1';

end process;

testDev: RippleAdder
Port map( A => tb_A,
          B => tb_B,
          Cin => tb_C,
          Cout => Cout,
          S => S);

end Behavioral;
```

SCHEMATIC

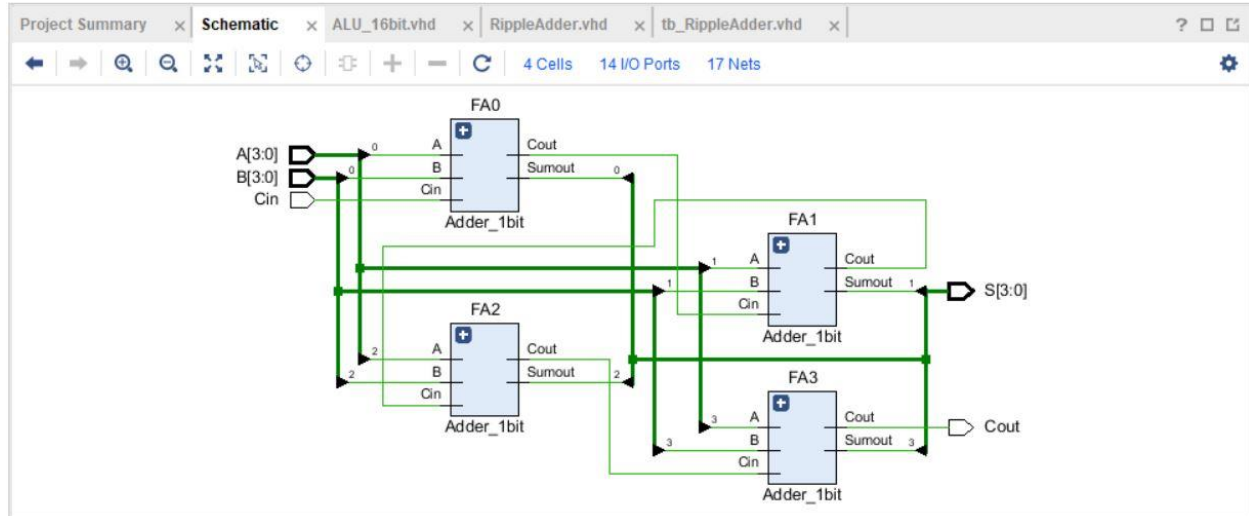


Fig. 3: Ripple Carry Adder showing four 1 bit Adders

SIMULATION



Fig. 4: Simulation showing waveforms for A,B,Cin, Cout and S.

As seen in the above simulation wave, S produces the desired Sum and Cout, the desired Carry output.

LAB 2

Each of these components are discussed in the following sections.

1. DEBOUNCE

Due to being mechanical in nature, they are often the bane of existence for digital designers when not dealt with correctly. The problem lies in that mechanical nature. When the button is pushed or released the spring inside causes the contacts to behave like a damped oscillator, which creates spikes in the signal.

This means, in between a swap from '0' to '1' or LOW to HIGH or '1' to '0' or HIGH to LOW, the switch goes through a few meta stable stages in between. During these meta stable stages, the output value may fluctuate.

It looks something like this :

 


Fig 5. Switch Debouncing

DESIGN

 


Fig. 6 Block Diagram of a Debounce Circuit

When a state changes from '0' to '1', the circuit waits for 20 ms for the switch to come to a stable state, before finally changing the output of the debounce at '1'.

In order to do this, we set the count value to 2499999.

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity debounce is
    Port( clk : in STD_LOGIC;
          btn : in STD_LOGIC;
          dbnc : out STD_LOGIC);
end debounce;

architecture Behavioral of debounce is
    signal sh : std_logic_vector(1 downto 0) := "00";
    signal cnt_value : std_logic_vector(22 downto 0):=(others => '0');
begin
    process(clk,btn)
    begin
        if (rising_edge(clk)) then
            sh(1) <= sh(0);
            sh(0) <= btn;
            if (unsigned(cnt_value) < 2499999) then
                dbnc <= '0';
            end if;
        end if;
    end process;
end;
```

```

    if (sh(1) = '1') then
        cnt_value <= std_logic_vector(unsigned(cnt_value)+1);
    else
        cnt_value <= (others => '0');
    end if;
else
    dbnc <= '1';
    if(btn = '0') then
        dbnc <= '0';
        cnt_value <= (others => '0');
    end if;
end if;
end if;
end process;
end Behavioral;

```

VHDL Testbench

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tb_debounce is
end tb_debounce;

architecture Behavioral of tb_debounce is
    component debounce
        Port (clk: in std_logic;
              btn: in std_logic;
              dbnc: out std_logic );
    end component;
    signal tb_clk: std_logic := '0';
    signal tb_btn: std_logic := '0';
    signal tb_dbnc: std_logic := '0';
    begin
        devut: debounce port map(  clk => tb_clk,
                                   btn => tb_btn,
                                   dbnc => tb_dbnc);
        clock: process
        begin
            tb_clk <= '1';
            wait for 4 ns;
            tb_clk <= '0';
            wait for 4 ns;
        end process;
        button: process
        begin
            tb_btn <= '0';

```

```

wait for 200us;
tb_btn <= '1';
wait for 60ms;
tb_btn <= '1';
wait for 2ms;
tb_btn <= '1';
wait for 1ms;
tb_btn <= '0';
tb_btn <= '1';
wait for 22ms;
tb_btn <= '0';
wait for 1ms;
tb_btn <= '1';
wait for 50 ms;
end process;
end Behavioral;

```

Simulation Results

 


Fig 7. Simulation Waveform for Debounce

As seen in the simulation waveform above, the circuit waits for 20ms till the output is stable at '1'. After 20s, the output is pulled up to '1'. As soon a '0' is received, the output is pulled down to '0'.

2. MY_ALU

This component takes 3 inputs, A, B and Opcode and generates a 4 bit output ALUOut. The functionalities are based on the following table:

opcode	function	opcode	function
x"0"	$A + B$	x"8"	$A >>> 1$ (right shift arithmetic)
x"1"	$A - B$	x"9"	not A
x"2"	$A + 1$	x"A"	A and B
x"3"	$A - 1$	x"B"	A or B
x"4"	$0 - A$	x"C"	A xor B
x"5"	$A > B$ (greater than - see note)	x"D"	A xnor B
x"6"	$A << 1$ (left shift logical)	x"E"	A nand B
x"7"	$A >> 1$ (right shift logical)	x"F"	A nor B

Fig. 8: Functionality Table

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity MY_ALU is
  Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
        B : in STD_LOGIC_VECTOR (3 downto 0);
        Opcode : in STD_LOGIC_VECTOR (3 downto 0);
        ALUOut : out STD_LOGIC_VECTOR (3 downto 0));
end MY_ALU;
```

architecture Behavioral of MY_ALU is

```
begin
opcodeselect:process(A,B,opcode)
begin
case opcode is
  when "0000" => ALUOut <= std_logic_vector(unsigned(A) + unsigned(B));
  when "0001" => ALUOut <= std_logic_vector(unsigned(A) - unsigned(B));
  when "0010" => ALUOut <= std_logic_vector(unsigned(A) + 1);
  when "0011" => ALUOut <= std_logic_vector(unsigned(A) - 1);
  when "0100" => ALUOut <= std_logic_vector(0 - unsigned(A));
```

```

when "0101" =>
  if A > B then
    ALUOut <= "0001";
  else
    ALUOut <= "0000";
  end if;
when "0110" => ALUOut <= std_logic_vector(unsigned(A(2 downto 0)) & '0');
when "0111" => ALUOut <= std_logic_vector('0' & unsigned(A(3 downto 1)));
when "1000" => ALUOut <= std_logic_vector(A(3) & unsigned(A(3 downto 1)));
when "1001" => ALUOut <= std_logic_vector(not (unsigned(A)));
when "1010" => ALUOut <= std_logic_vector(unsigned(A) and unsigned(B));
when "1011" => ALUOut <= std_logic_vector(unsigned(A) or unsigned(B));
when "1100" => ALUOut <= std_logic_vector(unsigned(A) xor unsigned(B));
when "1101" => ALUOut <= std_logic_vector(unsigned(A) xnor unsigned(B));
when "1110" => ALUOut <= std_logic_vector(unsigned(A) nand unsigned(B));
when "1111" => ALUOut <= std_logic_vector(unsigned(A) nor unsigned(B));
end case;
end process;

end Behavioral;

```

Schematic

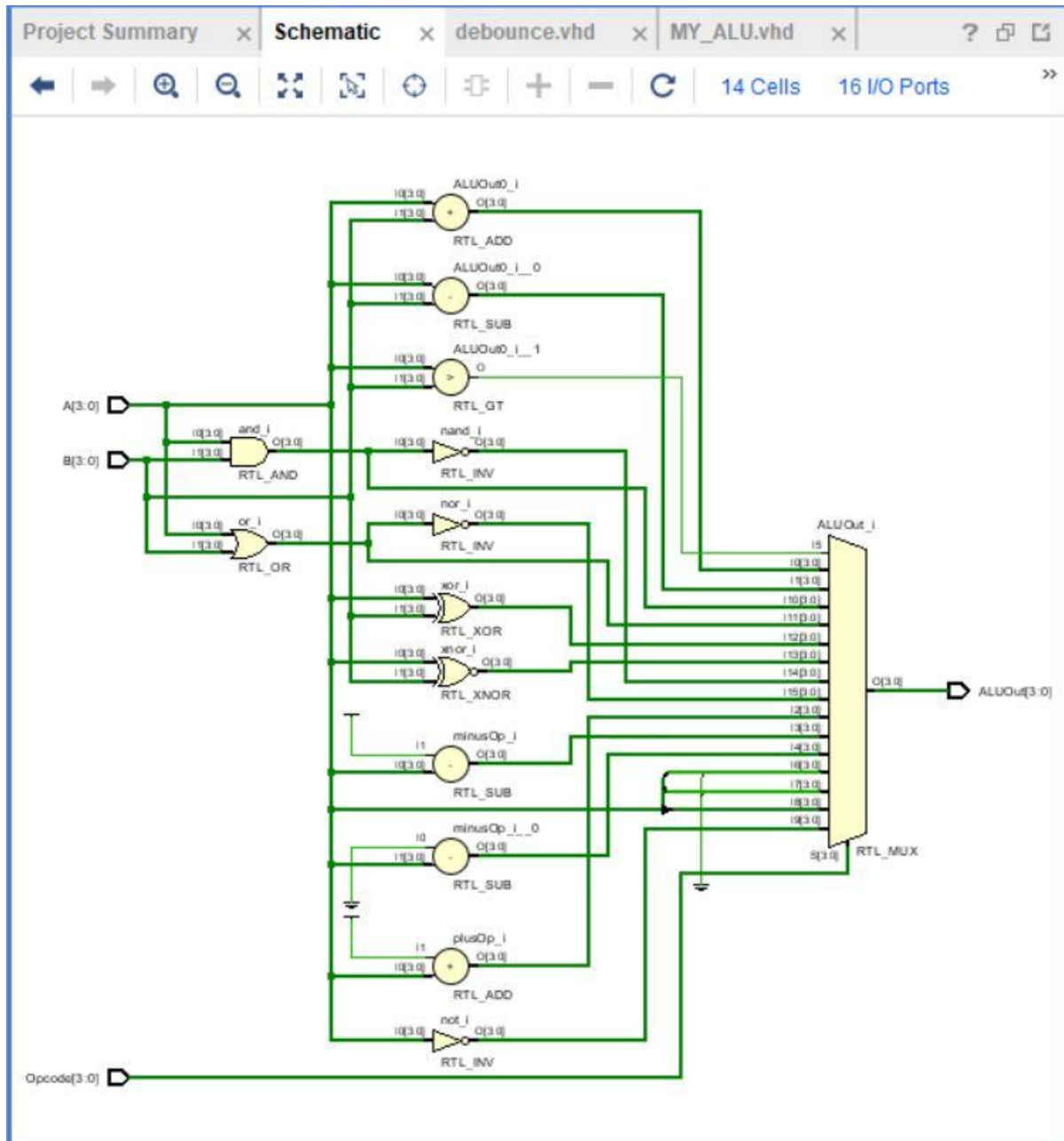


Fig. 9: My ALU Schematic

3. ALU_Tester

The top level synth only combines all available and pre made devices/ systems and creates instances of each component.

The intermediate wiring is done using locally created signals.

The ALU_Tester uses MY_ALU and Debounce as components. The debounce is used to assign functionalities to buttons.

BTN0 : LOAD A

BTN1 : LOAD B

BTN2 : LOAD OPCODE

BTN3 : RESET

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ALU_Tester is
    Port ( led : out STD_LOGIC_VECTOR (3 downto 0);
          btn : in STD_LOGIC_VECTOR (3 downto 0);
          sw : in STD_LOGIC_VECTOR (3 downto 0);
          clk : in STD_LOGIC);
end ALU_Tester;

architecture Behavioral of ALU_Tester is
    signal debounced: std_logic_vector(3 downto 0);
    signal temp_A, temp_b, temp_op, temp_reset: std_logic_vector(3 downto 0);

    component MY_ALU
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          Opcode : in STD_LOGIC_VECTOR (3 downto 0);
          ALUOut : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    component debounce
    Port( clk : in STD_LOGIC;
          btn : in STD_LOGIC;
          dbnc : out STD_LOGIC);
    end component;
begin

    assign:Process(clk)
```



```

begin
    if(rising_edge(clk)) then
        if(debounced(3) = '1') then
            temp_a <= "0000";
            temp_b <= "0000";
            temp_op <= "0000";
        elsif(debounced(0) = '1') then
            temp_b <= sw(3 downto 0);
        elsif(debounced(1) = '1') then
            temp_a <= sw(3 downto 0);
        elsif(debounced(2) = '1') then
            temp_op <= sw(3 downto 0);
        end if;
    end if;
end process;

Button_Debounce0: debounce
port map(clk => clk,
        btn => btn(0),
        dbnc => debounced(0));

Button_Debounce1: debounce
port map(clk => clk,
        btn => btn(1),
        dbnc => debounced(1));

Button_Debounce2: debounce
port map(clk => clk,
        btn => btn(2),
        dbnc => debounced(2));

Button_Debounce3: debounce
port map(clk => clk,
        btn => btn(3),
        dbnc => debounced(3));

ALU: MY_ALU
port map(A(3 downto 0) => temp_A(3 downto 0),
        B(3 downto 0) => Temp_B(3 downto 0),
        opcode(3 downto 0) => Temp_op(3 downto 0),
        ALUOut(3 downto 0) => led(3 downto 0));

end Behavioral;

```

Schematic

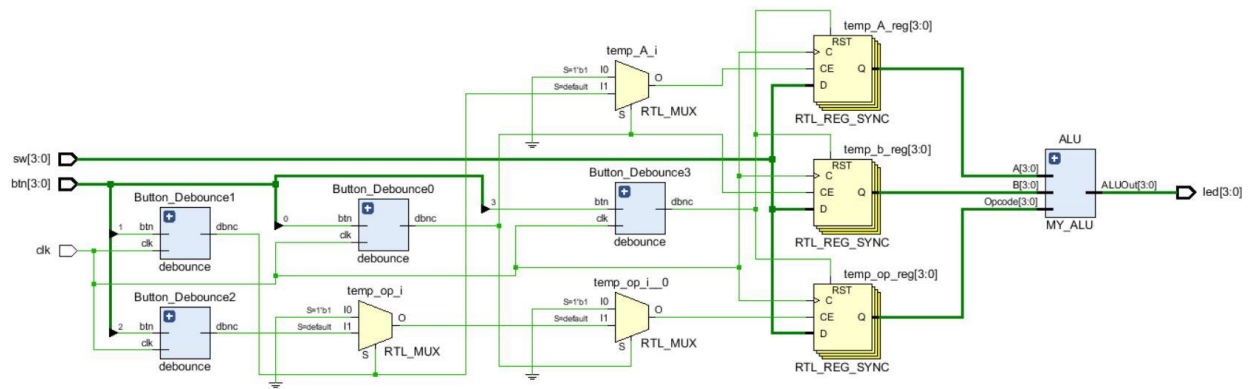


Fig. 10: ALU Tester Schematic

Post-Synthesis Schematic

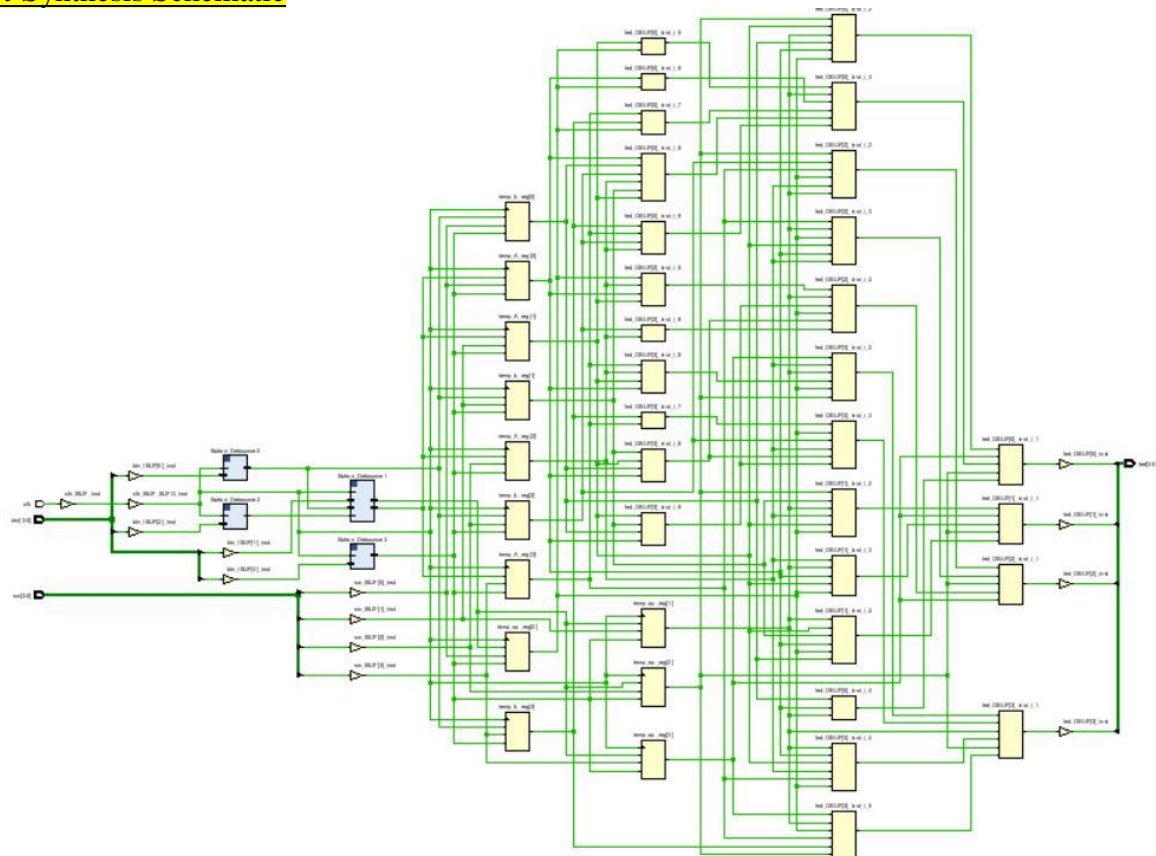


Fig. 11: Post Synthesis Schematic of ALU Tester

Implemented Design

 


Fig 12. Implemented Design showing the part of FPGA used to implement the ALU

Resource Utilization

Q Hierarchy

Name	Slice LUTs (17600)	Slice Registers (35200)	Slice (440 0)	LUT as Logic (17600)	LUT Flip Flop Pairs (17600)	Bonded IOB (100)	BUFGCTRL (32)
ALU_Tester	68	112	55	68	5	13	1
Button_Debounce0 (d...	11	25	13	11	1	0	0
Button_Debounce1 (d...	12	25	13	12	1	0	0
Button_Debounce2 (d...	11	25	11	11	1	0	0
Button_Debounce3 (d...	11	25	12	11	1	0	0

Fig. 13: Table showing Resources utilized in making the ALU

Power Utilization

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.096 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.1°C
 Thermal Margin: 58.9°C (5.0 W)
 Effective θ_{JA} : 11.5°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

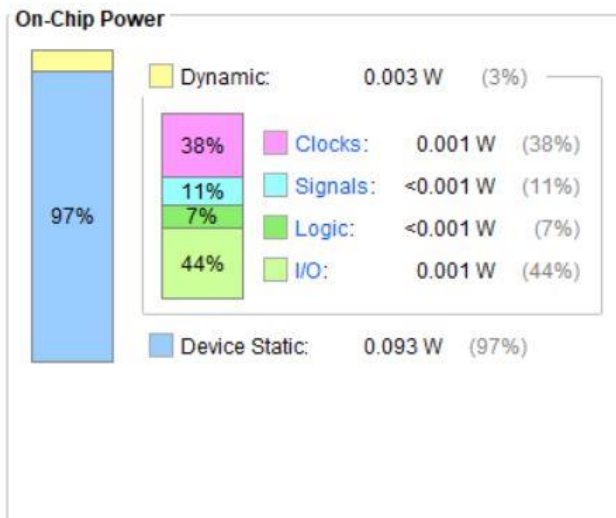


Fig. 14: Power Utilization Report Summary

Discussion

Observations

1. In the XDC file, while using multiple switches/leds/buttons we use '[' to denote each bit. While in the VHDL source files, we use '('.
2. A conditional in the code is converted into a MUX.
3. Any register that stores a value is represented as a D Flip Flop.
4. All inputs and outputs have buffers.
5. Overall Power Utilization for my design is 0.096 Watts, which can be further reduced by using a DSP Slice.
6. A total of 68 LUTs out of a 17600 are used for this design.

Questions/ Follow Up:

Concepts Understood:

1. Switches, Buttons, LEDs
2. Debouncing
3. Instantiation of components

Concepts Unsure of:

1. Why do we not debounce a switch when it is pulled down?
2. Can we implement pipelining on this design?
3. How can we differentiate our design from the existing designs?